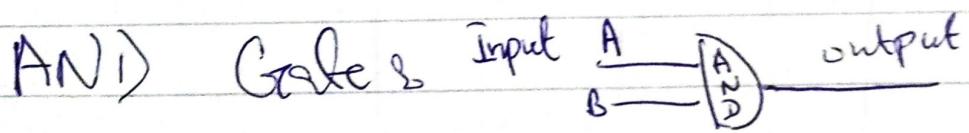



## DLD #01



Truth table is  $2^2 \Rightarrow$  base = 2-binary digits - 1,0  
power = number of inputs

$\Rightarrow 2^2 = 4 \Rightarrow$  number of entries in table

A	B	O/P	Table always starts from 0
0	0	0	
0	1	0	
1	0	0	$2^2 = 4/2 = 2$
1	1	1	$2/2 = 1$

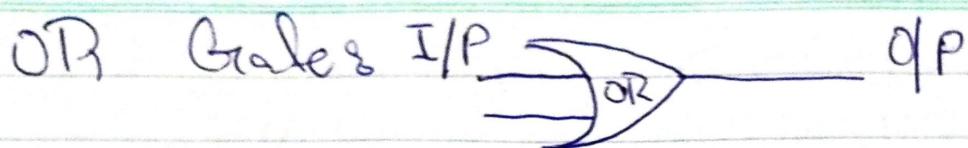

for example there are 4 ~~examples~~ inputs  
then,  $2^4 = 16 \Rightarrow$  entries


$$16/2 = 8 \Rightarrow 8 \text{ (0s and 1s)}$$

$$\begin{matrix} 8/2 = 4 \\ 4/2 = 2 \\ 2/2 = 1 \end{matrix}$$

	A	B	C	D	O/P
1.	0	0	0	0	0
2.	0	0	0	1	1
3.	0	0	1	0	1
4.	0	0	1	1	1
5.	0	1	0	0	1
6.	0	1	0	1	1
7.	0	1	1	0	1
8.	0	1	1	1	1
9.	1	0	0	0	1
10.	1	0	0	1	1
11.	1	0	1	0	1
12.	1	0	1	1	1
13.	1	1	0	0	1
14.	1	1	0	1	1
15.	1	1	1	0	1
16.	1	1	1	1	1


## LAB #02

→ Not Gates

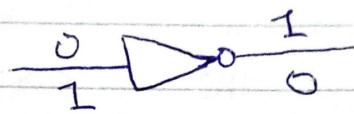

Universal gates & NAND & NOR

→ NAND Gate &

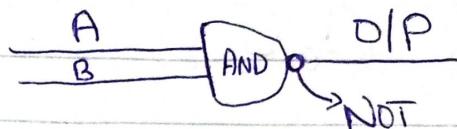


A	B	AND	O/P
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

∴ Reverse of AND

$$A'B' + A'B + AB'$$

→ NOR Gate &

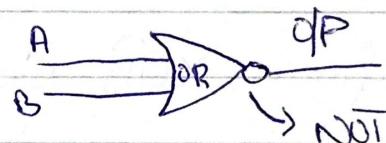


A	B	OR	O/P
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

∴ Reverse of OR

→ XOR Gate & (Exclusive OR Gate) =  $A \oplus B$

A	B	O/P
0	0	0
0	1	1
1	0	1
1	1	0

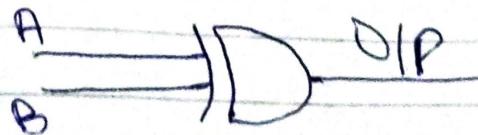∴ Output will be zero  
when two same bits



To make the expression from the truth table, we will consider only 1s output. Take complement on the 0 input.

XNOR Gate 2

A	B	O/P		row 1	row 4
0	0	1	✓	$A'B' + A'B$	
0	1	0			
1	0	0	✓		
1	1	1	✓		

Expression for XOR Gate 2

A	B	O/P
0	0	0
0	1	1
1	0	1
1	1	0

$$f = A'B + B'A$$

For Multiplication & AND Gate / IC

for Addition & OR Gate / IC

# DCD LAB #04

⇒ Random Custom Truth-table &

A	B	(O/P) → your choice
0	0	1 ↘
0	1	0
1	0	1 ↘
1	1	1 ↘

$$\Rightarrow F = A'B' + A'B + AB$$

Inputs  $2^n \Rightarrow 2^2 \Rightarrow 4$  entries in K-map

K-Map 2

	B	0	1
A			
0	00	01	
1	10	11	

⇒ Now implement the equation into K-map to reduce it.

$$\Rightarrow F = \frac{A'B'}{(00)} + \frac{A'B}{(01)} + \frac{AB}{(11)}$$

	B	0	1
A			
0	1	1	
1			1

Now, next step is pairing from K-map.

	B	0	1
A			
0	1	1	
1		1	

pair overlapping is allowed.

Now, look at which variable is constant in a pair, not in the

Block, but outside the block, that are row and column.

In the first pair where the row of A is constant, that is 0.

So,  $F = A'$  and in the second pair, the column (B) is constant, 1

So,  $F = A' + B$  well done! expression is reduced.

It is give the same answer as that of the original equation.

$\Rightarrow$  Random Equation of your choice

$$\Rightarrow 3 \text{ inputs} \Rightarrow F = ABC' + AB'C' \\ + ABC + A'B'C' + A'B'C$$

Now, K-mapping  $\Rightarrow 2^n \Rightarrow n = \text{number of inputs}$

$2^3 \Rightarrow 8$  entries/blocks in K-map.

A	B	C	00	01	11	10
0	0	0	000	001	011	010
1	1	0	100	101	111	110

← Gray Code & LSB  
will change, one bit at a time.

421

Used sequence is

$$00 \rightarrow 0$$

$$01 \rightarrow 1$$

$$10 \rightarrow 2$$

$$11 \rightarrow 3$$

⇒ But gray don't follow this, if only changes one bit at a time of LSB (Least significant Bit)

Now, map the equation to

$$\begin{aligned} & \text{F} = \frac{(010)}{A'BC'} + \frac{(100)}{AB'C'} + \frac{(111)}{ABC} + \frac{(000)}{A'B'C'} \\ & + \frac{(001)}{A'B'C} \end{aligned}$$

		A'BC	00	01	11	10
		0	1	1		1
		1	1		1	

$$\Rightarrow F = B'C' + A'B' + ABC + A'B'C'$$

⇒ Write the single / non-pair elements as it is.

# TASK #01



$$F = A'B'C' + A'B'C + A'BC' + AB'C + ABC' \\ + ABC + AB'C'$$

$\Rightarrow 2^n = 2^3 = 8$  entries

A	B	C	O/P
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1


$$\Rightarrow F = \frac{A'B'C'}{(000)} + \frac{A'B'C}{(001)} + \frac{A'BC'}{(010)} + \frac{AB'C}{(101)} \\ + \frac{ABC'}{(110)} + \frac{ABC}{(111)} + \frac{AB'C'}{(100)}$$

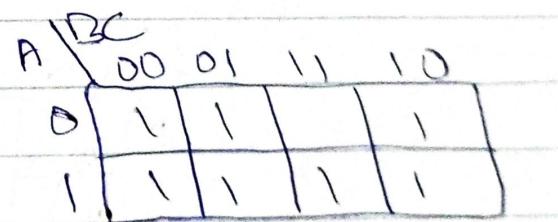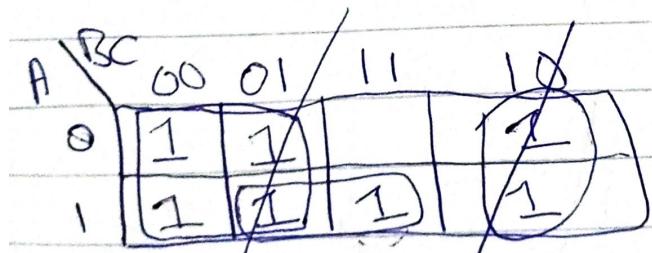K-map  $\Rightarrow 2^n \Rightarrow 2^3 = 8$  blocks in K-map



$$\Rightarrow F = B' + AC + BC'$$

$F = B' + A + C'$

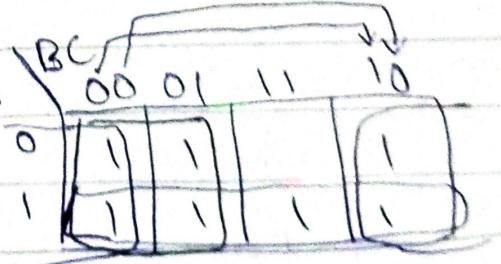



# Task # 02

Truthtable  $\rightarrow$  Random &

A	B	C	O/P
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1 ✓
1	0	0	1 ✓
1	0	1	1 ✓
1	1	0	1 ✓
1	1	1	1 ✓

$$\begin{aligned} \text{Equation s } F = & \frac{(011)}{A'B'C} + \frac{(100)}{AB'C'} + \frac{(101)}{ABC'} \\ & + \frac{ABC'}{(110)} + \frac{ABC}{(111)} \end{aligned}$$

$$2^3 = 8 \text{ blocks}$$

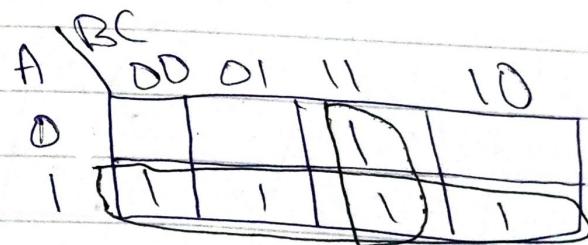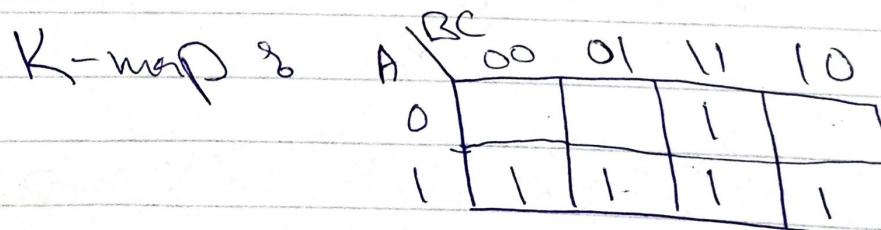

Pairing &

$$f = A + BC$$

# DCD LAB #05

## Adders &

⇒ Half Adders &

Equations of,

$$\text{Sum} = \underbrace{A'B + AB'}_{\text{so } \text{XOR} = A \oplus B}$$

$$\text{Carry} = AB$$

A	B	Sum	Carry
0	0	0	0
0	1	1 ✓	0
1	0	1 ✓	0
1	1	0	1 ✓

## Full Bit Adder &

A	B	Cin	Sum	Carry
0	0	0	0	0
0	0	1	1 ✓	0
0	1	0	1 ✓	0
0	1	1	0	1
1	0	0	1 ✓	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1 ✓	1

$$\begin{aligned} \text{Sum} = & A'B'Cin + A'BCin' \\ & + AB'Cin' + ABCin \end{aligned}$$

$$\Rightarrow \text{Sum} = A' \underbrace{(B'C_{in} + BC_{in}')}_{B} + A \underbrace{(B'C_{in}' + BC_{in})}_{B'} \\ \text{XOR} \qquad \qquad \qquad \text{XNOR}$$

$$\Rightarrow B = \text{XOR} = B'C_{in} + BC_{in}' = B \oplus C_{in}$$

$$\Rightarrow B' = \text{XNOR} = B'C_{in}' + BC_{in} = \overline{B \oplus C_{in}}$$

$$\begin{aligned} \Rightarrow \text{Sum} &= A'B + AB' \\ &= A \oplus B \\ &= A \oplus B \oplus C_{in} \end{aligned}$$

$$\begin{aligned} \Rightarrow \text{Carry} &= A'BC + AB'C + ABC' + ABC \\ &= C(A'B + AB) + AB(C' + C) \\ &\quad \text{XOR} = A \oplus B \qquad \qquad \qquad 0+1=1 \\ &= C(A \oplus B) + AB \\ &= C(A \oplus B) + AB \end{aligned}$$

9/1  
Osama Bin Laden

# DLD LAB #06

## "Subtractors"

Half subtractors

$$\begin{aligned} \text{Difference} &= A'B + B'A \\ &= A \oplus B \end{aligned}$$

A	B	Diff	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

$$\Rightarrow \text{Borrow} = A'B$$

Full Subtractors

A	B	C	Difference	Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$\begin{aligned} \text{Diff} &= A'B'C + A'BC' + AB'C' + ABC \\ &= A'(\underline{B'C + BC'}) + A(\underline{B'C' + BC}) \\ &\quad \text{XOR} \qquad \qquad \qquad \text{XNOR} \end{aligned}$$

$$\text{XOR} = B'C + BC' = \underline{\underline{B \oplus C}}$$

$$\text{XNOR} = B'C' + BC = \overline{B \oplus C}$$

let  $B \oplus C = X$ ,  $\overline{B \oplus C} = X'$

$$\begin{aligned}\text{diff} &= A'X + AX' \quad \therefore A \otimes X = \text{XOR} \\ &= A \oplus X \quad \therefore X = B \oplus C \\ &= A \oplus B \oplus C\end{aligned}$$

$$\begin{aligned}\text{Borrow} &= A'B'C + A'BC' + A'BC + ABC \\ &= A \underbrace{(B'C + BC')}_{\text{XOR}} + BC \underbrace{(A' + A)}_{0+1=1} \\ &= A'(B \oplus C) + BC\end{aligned}$$

LAB # 07

Comparatives  $\rightarrow$  1-Bit

Input		Output		
A	B	$Y_1 = (A < B)$	$Y_2 (A = B)$	$Y_3 (A > B)$
0	0	0	1 $\rightleftharpoons$	0
0	1	1 $\rightleftharpoons$	0	0
1	0	0	0	1 $\rightleftharpoons$
1	1	0	1 $\rightleftharpoons$	0

# LAB # 07

Equations  $\rightarrow$

$$Y_1 = A'B \quad Y_2 = A'B' + AB \\ Y_3 = AB' \quad = \underline{\underline{A \oplus B}}$$

2-Bit  $\Rightarrow$

2-bit.  $A = A_1, A_0$ ,  $B = B_1, B_0$

$A_1$	$A_0$	$B_1$	$B_0$	$Y_1(A < B)$	$Y_2(A=B)$	$Y_3(A > B)$
0	0	0	0	0	1 ✓	0
0	0	0	1	1 ✓	0	0
0	0	1	0	1 ✓	0	0
0	0	1	1	1 ✓	0	0
0	1	0	0	0	0	1 ✓
0	1	0	1	0	1 ✓	0
0	1	1	0	1 ✓	0	0
0	1	1	1	1 ✓	0	0
1	0	0	0	0	0	1 ✓
1	0	0	1	0	0	1 ✓
1	0	1	0	0	1 ✓	0
1	0	1	1	1 ✓	0	0
1	1	0	0	0	0	1 ✓
1	1	0	1	0	0	1 ✓
1	1	1	0	0	0	1 ✓
1	1	1	1	0	1 ✓	0

∴ 2-Bit  $\Rightarrow A=2^1 < B=2^1$

$$0 \ 1 < 1 \ 0$$

$$\text{Equation 2} \quad Y_1 = A_1' A_0' B_1' B_0 + A_1' A_0' B_1 B_0' + \\ A_1' A_0' B_1 B_0 + A_1' A_0 B_1 B_0' + \\ A_1' A_0 B_1 B_0 + A_1 A_0' B_1 B_0$$

$$\Rightarrow Y_2 = A_1' A_0' B_1' B_0' + A_1' A_0 B_1' B_0 + A_1 A_0' B_1' B_0' \\ + A_1 A_0 B_1 B_0$$

$$\Rightarrow Y_3 = A_1' A_0 B_1' B_0' + A_1 A_0' B_1' B_0 + A_1 A_0' B_1 B_0' + \\ A_1 A_0 B_1' B_0' + A_1 A_0 B_1' B_0 + A_1 A_0 B_1 B_0'$$

K-mapping 3

		B <sub>1</sub>	B <sub>0</sub>			
			00	01	11	10
		A <sub>1</sub> A <sub>0</sub>	00	01	11	10
	00		1	1	1	
	01			1	1	
	11					
	10				1	

$$Y_1 = A_1' B_1 + A_1' A_0' B_0 + A_0' B_1 B_0$$

		B <sub>1</sub>	B <sub>0</sub>			
			00	01	11	10
		A <sub>1</sub> A <sub>0</sub>	00	01	11	10
	00		1			
	01			1		
	11				1	
	10					1

\$\Rightarrow\$ Not possible  
no pairs


$$Y_3 = A' B' D_0 + A' B D_1 + A' B' D_2 + A' B D_3 + A B' D_0 + A B D_1 + A B' D_2 + A B D_3$$

	$A'$	$B'$	$D_0$	$D_1$	$D_2$	$D_3$
$A'$	00	00	00	01	11	10
$B'$	00	01	11	10	11	00
$A$	00	01	11	10	00	01
$B$	01	11	10	00	01	11

$$Y_3 = A_1 B_1' + A_0 B_1 B_0' + A_1 A_0 B_0'$$

$L_{AB} \neq 08$      $\therefore 74LS138 = \text{Decoder}$   
 $\therefore 74LS148 = \text{Encoder}$

Decoders 2 to 4 lines &

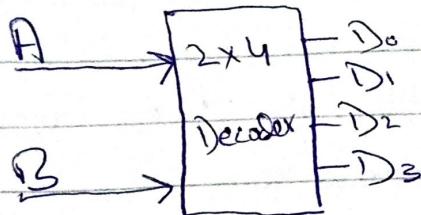


		inputs		outputs			
		A	B	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>
		0	0	1	0	0	0
		0	1	0	1	0	0
		1	0	0	0	1	0
		1	1	0	0	0	1

$$\begin{matrix} 2 \text{ to } 4 \\ \text{inputs} \end{matrix} : 2^2 = 2^2 = 4 \quad \begin{matrix} \text{outputs} \end{matrix}$$

$$\begin{aligned} D_0 &= A'B' & D_1 &= A'B \\ D_2 &= AB' & D_3 &= AB \end{aligned}$$

Decoders 3 to 8 lines &

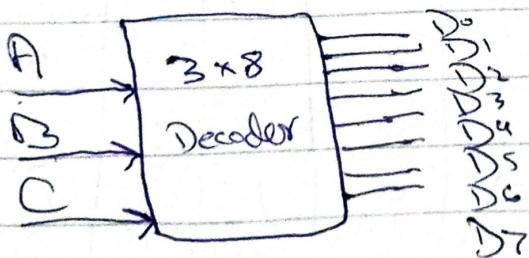

inputs			$Y_0$	$Y_1$	$Y_2$	$Y_3$	$Y_4$	$Y_5$	$Y_6$	$Y_7$
A	B	C	$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	1	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	0	1	0
1	1	0	0	0	0	0	0	0	0	1
1	1	1	0	0	0	0	0	0	0	1

$$D_0 = A'B'C'$$

$$D_1 = A'B'C$$

$$D_2 = A'BC'$$

$$D_3 = A'BC$$

$$D_4 = ABC'$$

$$D_5 = ABC$$

$$D_6 = AB'C'$$

$$D_7 = ABC$$

Encoders 8 to 3 & It is the reverse  
of decoders.


$\Rightarrow 74LS148 = IC$

inputs								output		
$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$	X	Y	Z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

$$X = D_4 + D_5 + D_6 + D_7$$


$$Y = D_2 + D_3 + D_6 + D_7$$

$$Z = D_1 + D_3 + D_5 + D_7$$

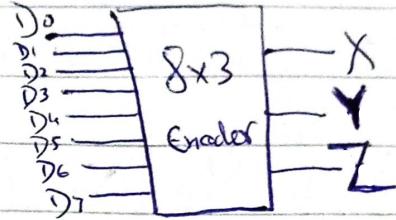

LAB # 09

$\Rightarrow 4 \times 1$  Mux 2

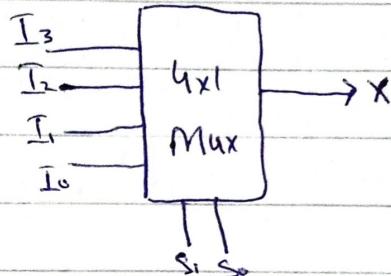

S <sub>1</sub>	S <sub>0</sub>	X
0	0	I <sub>0</sub>
0	1	I <sub>1</sub>
1	0	I <sub>2</sub>
1	1	I <sub>3</sub>


$\Rightarrow$  4 inputs & 1 output

$\Rightarrow S_1$  &  $S_0$  = selection pins

$\Rightarrow$  74LS153 (mux) 4 inputs

$\Rightarrow 8 \times 1$  Mux 2

C	B	A	X
S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>	
0	0	0	I <sub>0</sub>
0	0	1	I <sub>1</sub>
0	1	0	I <sub>2</sub>
0	1	1	I <sub>3</sub>
1	0	0	I <sub>4</sub>
1	0	1	I <sub>5</sub>
1	1	0	I <sub>6</sub>
1	1	1	I <sub>7</sub>

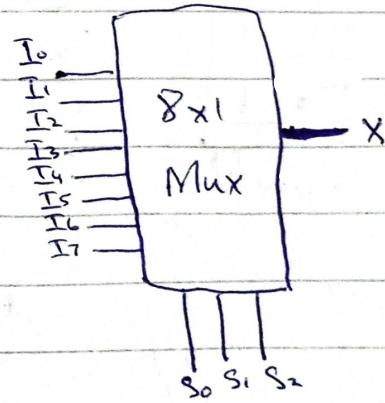


$\Rightarrow$  74LS151 (Mux)

8 input pins

$\Rightarrow$  In trainer, checks first four pins, and then other four





De Multiplex  $\rightarrow 1 \times 4$

$S_1$	$S_0$	$X_3$	$X_2$	$X_1$	$X_0$	$I_o$
0	0	0	0	0	1	
0	1	0	0	1	0	
1	0	0	1	0	0	
1	1	1	0	0	0	

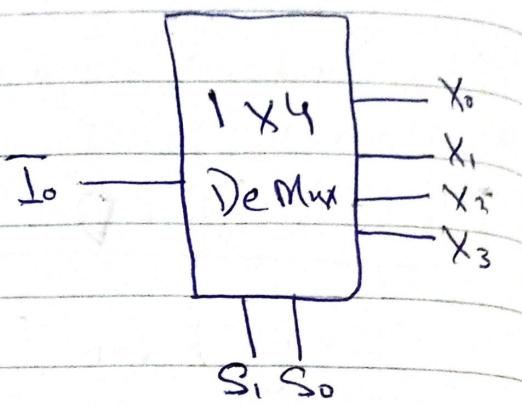

## LAB # 10

7 Segment Display  $\rightarrow$

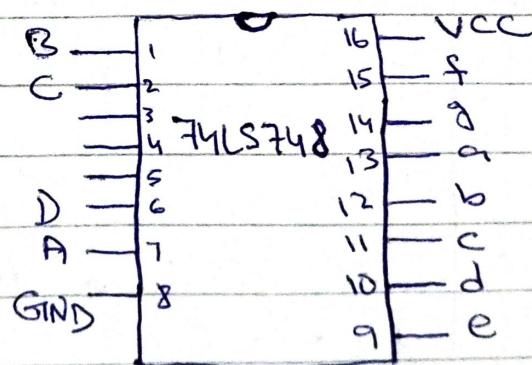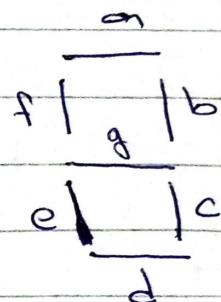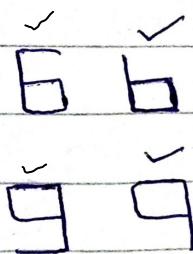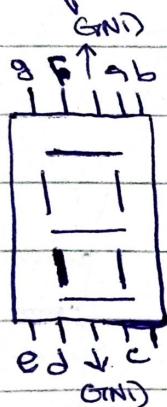

Inputs

Output

D	C	B	A	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0
2	0	0	1	0	1	1	0	1	0	1
3	0	0	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1
5	0	1	0	1	1	0	1	1	0	1
6	0	1	1	0	1	0	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0
8	1	0	0	0	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1


# LAB # 11

Latches & S.R. latch using NOR

NOR

A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

Sequential vs combinational

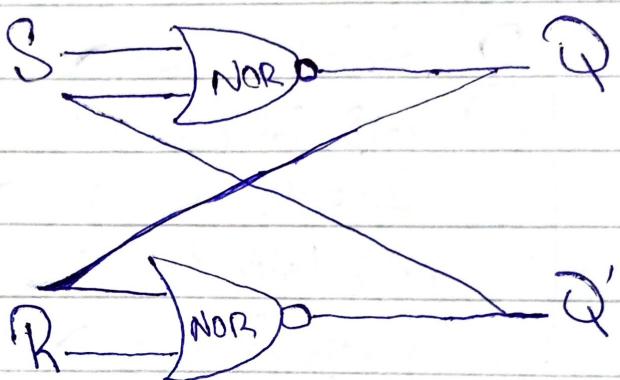


Inputs | Outputs  $\rightarrow$  Wrong Truth Table

S	R	Q	$Q'$
0	1	1	0 $\rightarrow$ Set State
0	0	1	0 $\rightarrow$ Hold Latched
1	0	0	1 $\rightarrow$ Reset State
0	0	0	1 $\rightarrow$ Hold Latched
1	1	0	0 $\rightarrow$ undefined

$\Rightarrow$  S.R. latch using NAND

NAND

A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

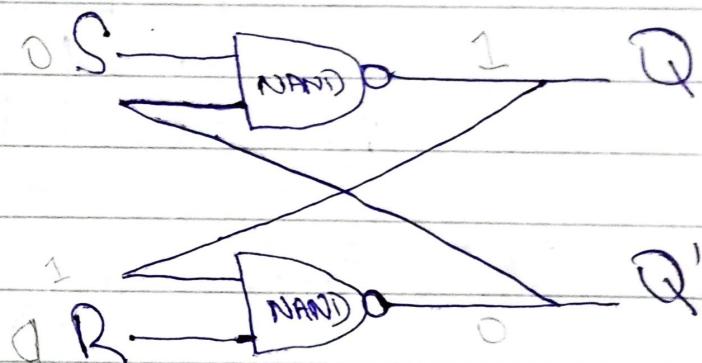


Correct Truth Table

Inputs		Output	
S	R	Q	$Q'$
0	1	1	0
0	0	1	0
1	0	0	1
0	0	0	1
1	1	0	0

Inputs		Output	
S	R	Q	$Q'$
0	1	1	0
0	0	1	0
1	0	0	1
0	0	0	1
1	1	0	0

# UAB #12

JK flip flops & (Sequential)

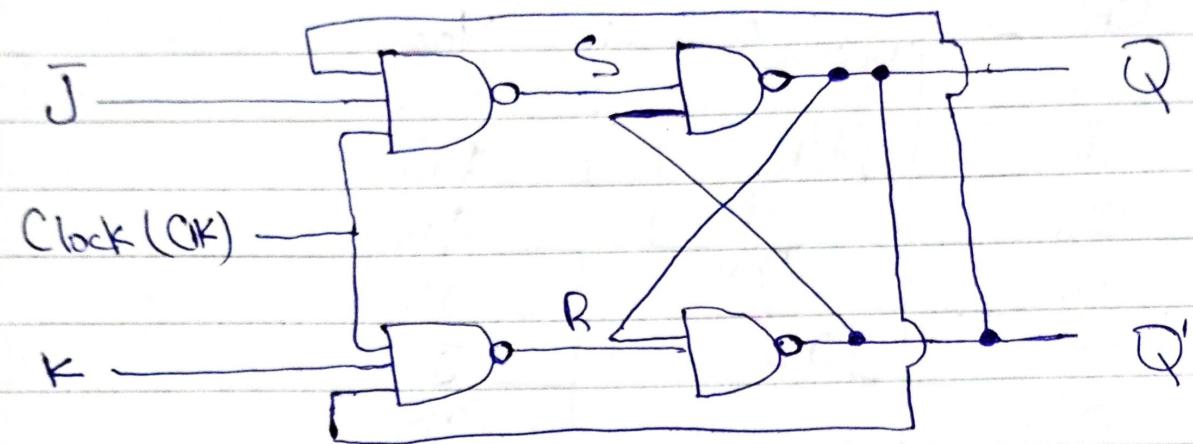

CLK	J	K	S	R	Q	$Q'$
0	X	X	1	1		
1	1	0	0	1	1	0
1	0	1	1	0	0	1
[1]	1	1	0	1	1	0
			1	0	0	1


Toggle

NAND

0	0	1
0	1	1
1	0	1
1	1	0


Use Pulse switches on  
trainer for clock A' or B'

Multisim  
74LS112

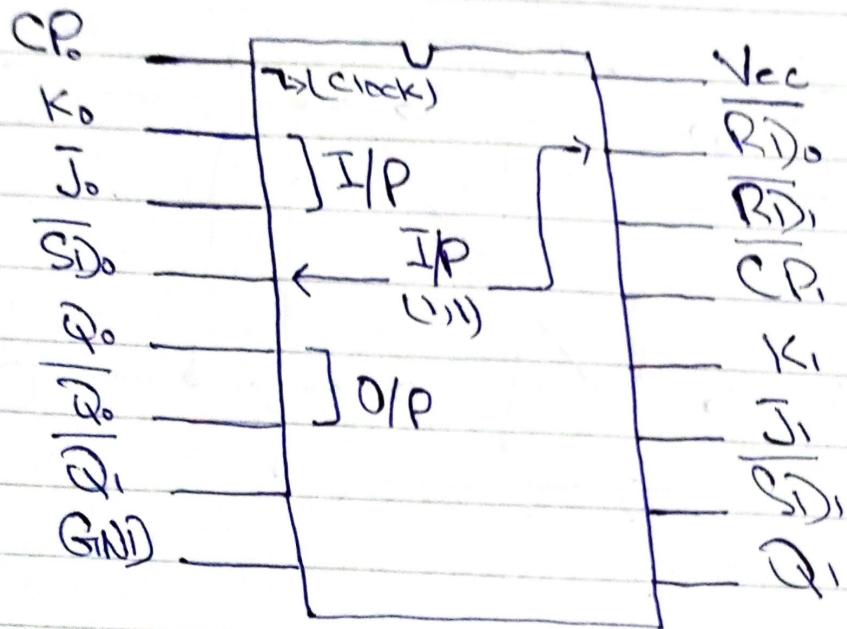


2-flip flops in one IC

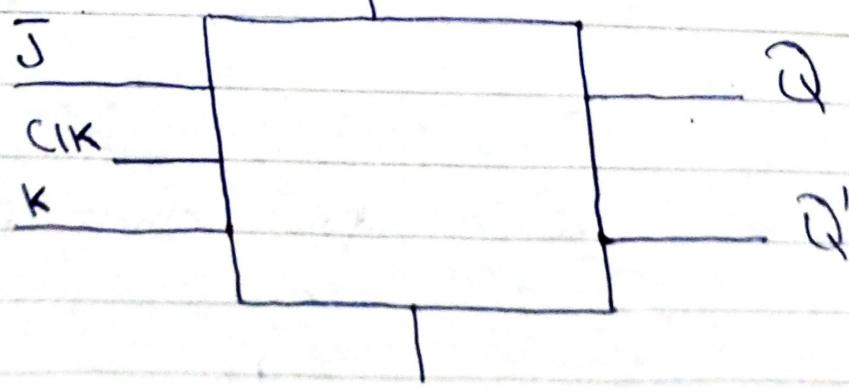$\Rightarrow$  JK flip flop?  
(Set) S<sub>0</sub> (0)




(Reset) R<sub>D</sub> (0)

T flip flops

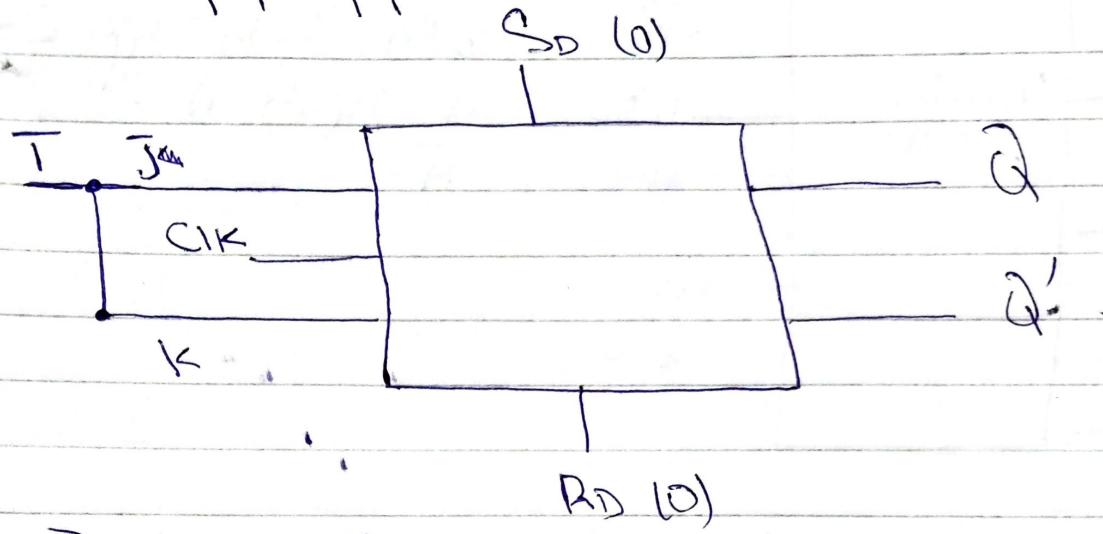


D flip flops

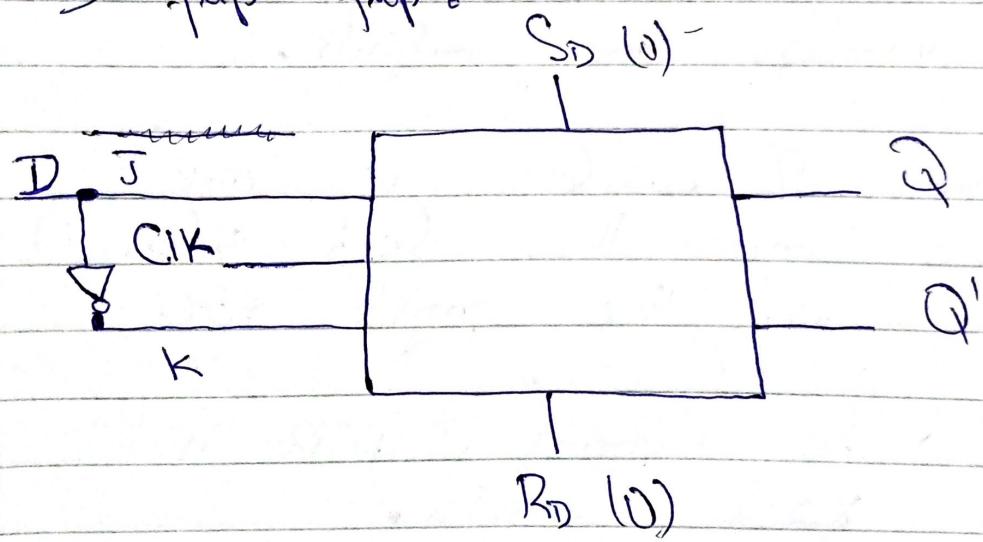

LAB # 13

Counters & 74LS393

→ 4-bit counter  
0-15 Decimal

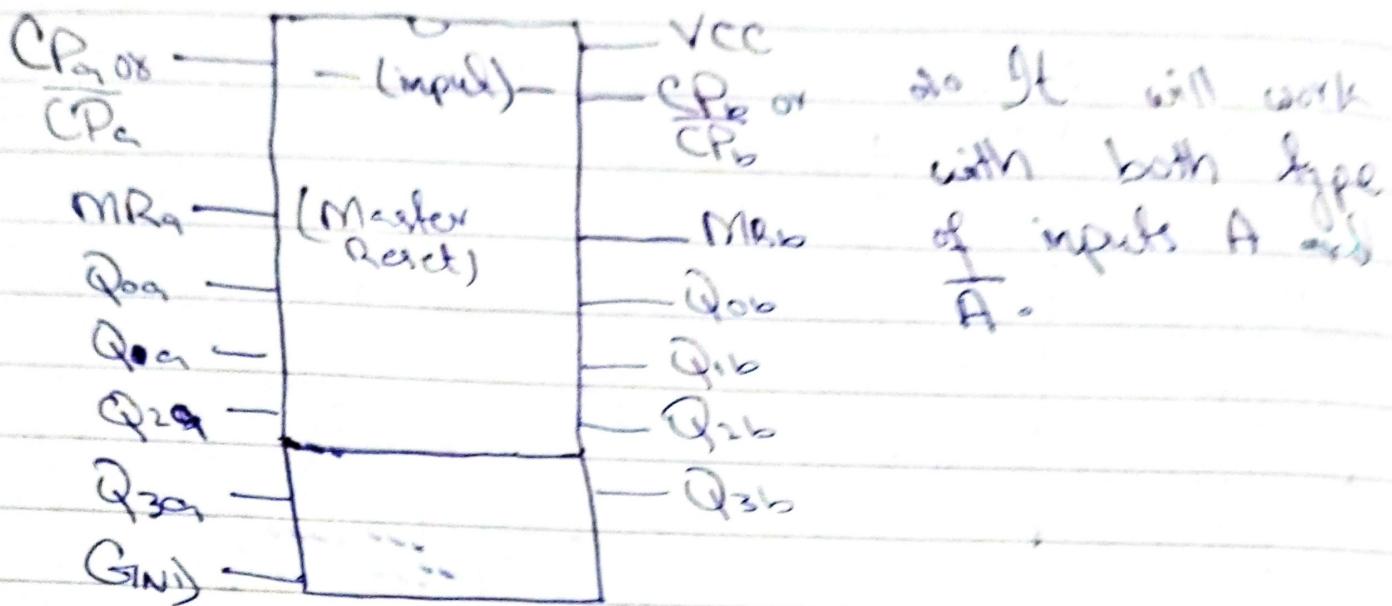

∴ CP is input; MR is master reset; Q<sub>0</sub>-Q<sub>3</sub> are outputs.


∴ There are 2-counters in one IC, one on the left side, the other on the right side.

∴ CP is to count, MR is used to reset counter.

## Shift Registers

S <sub>1</sub>	S <sub>0</sub>	D/P - Modes
0	0	No change
0	1	Right shift - one bit at a time
1	0	Left shift - a time
1	1	Parallel - 4-bits altogether

# 74LS194

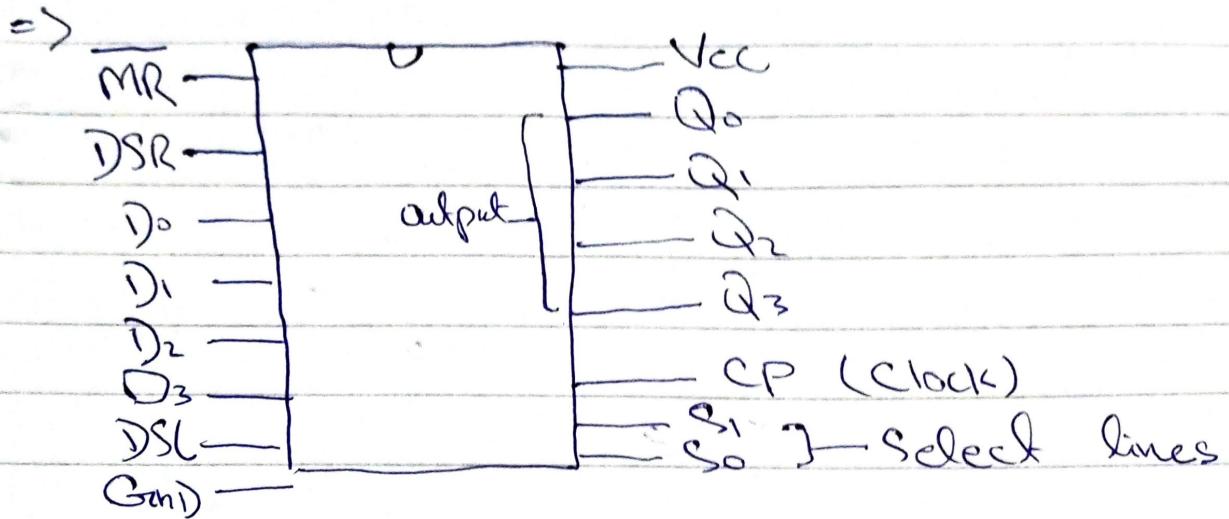

∴ DSR = Shift Right Input

∴ DSL = Shift Left Input

∴ D<sub>0</sub>-D<sub>3</sub> = Parallel inputs

Give clock for every input

=> Keep reset to HIGH so the box will make it LOW.